

2023

PHYSICS — HONOURS

Paper : CC-9

(Syllabus : 2019-2020)

(Analog Electronics)

Full Marks : 50

The figures in the margin indicate full marks.


*Candidates are required to give their answers in their own words
as far as practicable.*

Answer **question no. 1** and **any four** questions from the rest.

1. Answer **any five** questions :

2×5

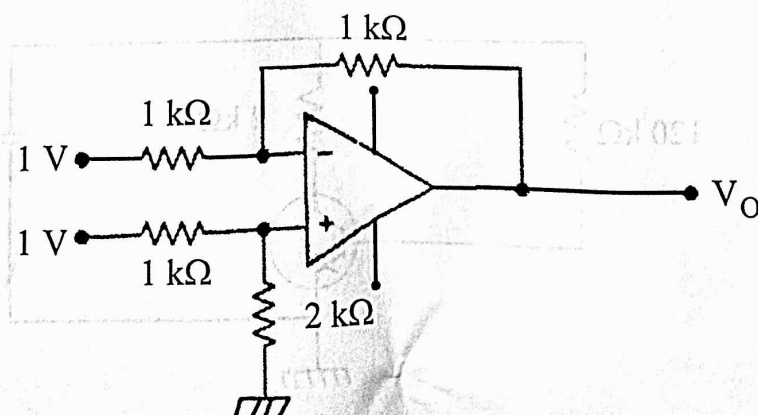- (a) State and explain Reciprocity theorem.
- (b) Why is there a reverse saturation current in a p-n junction? Does it vary with reverse bias and temperature?
- (c) Why is the base region least heavily doped in a BJT?
- (d) What do you mean by a pinch-off condition of JFET?
- (e) A BJT is a current controlled device and a FET is voltage controlled device. Explain.
- (f) Explain Barkhausen's criterion for self-sustained oscillation.
- (g) What is the output of the following circuit?




2. (a) State and explain Thevenin's theorem.

(b) State Superposition theorem.


(2)

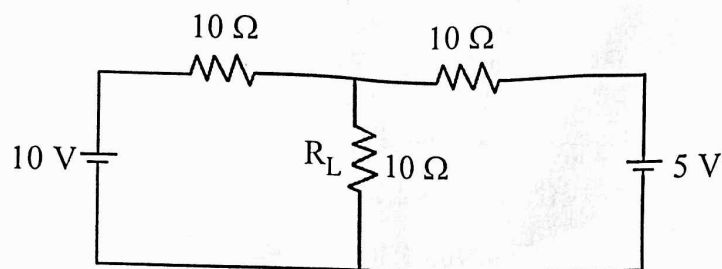- (c) Using superposition theorem, find current through R_L . Verify the current using Thevenin's theorem.



(2+1)+2+(3+2)

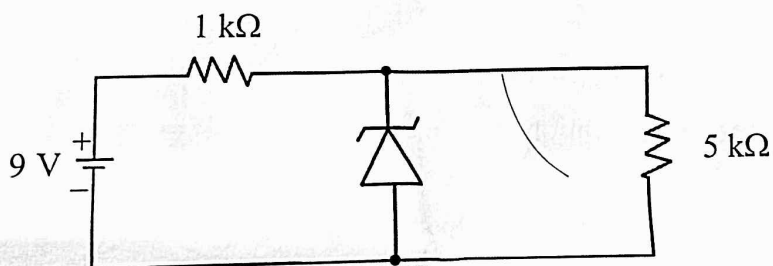
3. (a) A pure semiconductor has intrinsic current density of $10^{20}/\text{m}^3$ at 300K. When doped with donor type impurities, hole concentration decreases to $10^{18}/\text{m}^3$ at the same temperature. Find the value of electron density.
- (b) Draw the energy band diagram of an open circuited p-n junction.
- (c) In the circuit diagram, what are the currents flowing through $1\text{ k}\Omega$ and $5\text{ k}\Omega$ resistances and the Zener diode? What happens when the resistances are interchanged their positions? Breakdown voltage of Zener diode is 6.0 V .



- (d) Explain the principle of operation of a photodiode.

2+2+4+2

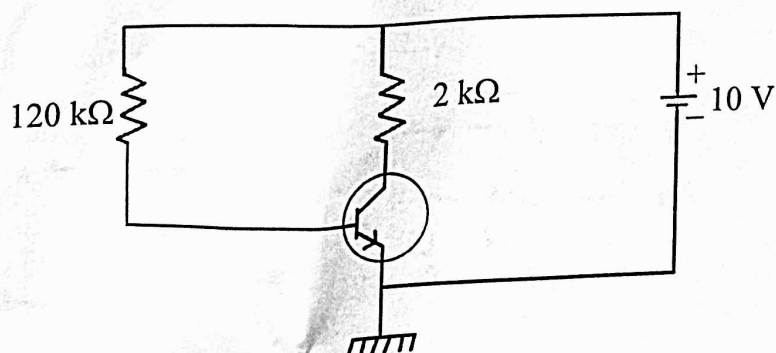4. (a) Define α and β of a transistor. Find the relation between them.
- (b) In the circuit, the transistor has $\beta = 100$. Determine the region of operation and the value of I_B , I_C and V_{CE} . Consider $V_{BE} = 0.7\text{ V}$.



- (c) Explain how self-bias circuit ensures stability of Q point.

(2+2)+4+2

5. (a) Explain how voltage gain is stabilized with the application of negative feedback.
- (b) The open loop gain of an amplifier is 100. What will be the overall gain when a negative feedback of 0.6 is applied to the amplifier?

(3)

Z(4th Sm.)-Physics-H/CC-9/CBCS
[Syllabus : (2019-20) & (2018-19)]

- (c) What is meant by threshold voltage of a MOSFET?
- (d) Draw the circuit diagram of a CS JFET amplifier. The load resistance, ac drain resistance and the transconductance of the JFET amplifier are $500\text{ k}\Omega$, $100\text{ k}\Omega$ and $0.2 \times 10^{-3}\text{ A/V}$ respectively. Obtain voltage gain of the amplifier. 2+2+2+(2+2)
6. (a) What is the significance of virtual ground in operational amplifier?
- (b) Draw the circuit diagram of Schmidt trigger and explain its operation.
- (c) A ramp voltage of 1.5 V/m is applied on an OP AMP differentiator with $R = 2\text{ k}\Omega$ and $C = 0.01\text{ }\mu\text{F}$. Find the output voltage.
- (d) Compare ideal and practical characteristics of OP AMP. 2+4+2+2
7. (a) A Wien bridge oscillator is to be constructed at frequency 10 kHz . If the capacitance of the circuit be 500 pF , find the resistance used in the circuit. Draw the necessary circuit diagram.
- (b) Explain briefly the function of Astable multivibrator and write down the expression for time period.
- (c) Write down the expression for frequency of a phase shift oscillator. What is the minimum value of gain of the amplifier for sustained oscillation? 3+4+3