

2023

PHYSICS — HONOURS

Paper : CC-13

(Syllabus : 2019-2020)

[Digital Electronics]

Full Marks : 50

The figures in the margin indicate full marks.


*Candidates are required to give their answers in their own words
as far as practicable.*

Answer **question no. 1** and **any four** questions from the rest.


1. Answer **any five** questions :

2×5

 - (a) What is monolithic IC?
- (b) Convert the hexadecimal number C1.A to a binary number.
- (c) Reduce the Boolean expression $Y = A\bar{B} + \bar{A}B + AB + \bar{A}\bar{B}$ in its simplest form.
- (d) Which logic gate can be used as parity checker? Explain.
- (e) Using 2's complement method subtract 00111 from 10101.
- (f) Write at least two differences between latches and flip-flops.
- (g) Write the Boolean expression for the output Y in the following figure and simplify it.



 2. (a) Draw the circuit diagram for realising AND gate using transistors.
- (b) In the following NOT gate, calculate the base resistance (R_B) and collector resistance (R_C).
[Given : $h_{FE} = 250$, $I_C(\text{Sat}) = 10 \text{ mA}$, $V_{CC} = 10 \text{ V}$ and $V_i = 0 \text{ to } 10 \text{ V}$]



Please Turn Over

(c) Perform the binary operations : $11111 + 1011 - 111$

Use 1's complement method for subtraction.

(d) What are the two advantages of higher density ICs?

2+3+3+2

3. (a) Simplify the following logic function in SOP form using K-map and implement it by using NAND gates only.

$$F(A, B, C, D) = \sum m(0, 2, 3, 5, 7, 8, 12, 13)$$

(b) Implement XOR gate using NOR gates only and give its truth table.

(c) Write two advantages of CMOS logic over TTL logic.

(3+2)+(2+1)+2

4. (a) Show that a full adder circuit can be realised using half adders and an OR gate.

(b) What is a demultiplexer? Draw the block diagram of a 4 to 16 line demultiplexer.

(c) Using a 3 to 8 decoder and an OR gate, draw the circuit diagram to realise the following Boolean functions simultaneously : $F_1(A, B, C) = \sum m(0, 4, 6)$ and $F_2(A, B, C) = \sum m(1, 2, 3, 7)$.

3+(1+2)+4

5. (a) Draw the circuit diagram of a clocked SR-Flip-flop. How does the trigger pulse controls the change of state of this flip-flop? Explain.

(b) Discuss the differences between D and T type flip-flops using block diagrams and truth-tables.

(c) Convert an SR flip-flop into a JK flip-flop. [circuit diagram only]

(2+2)+(2+2)+2

6. (a) Draw the block diagram of a 4-bit SISO shift register.

(b) The clock frequency is 2 MHz. How long will it take to serially load an 8-bit shift register?

(c) The bit sequence 0010 is serially entered (right most bit first) into a 4-bit parallel out left shift register that is initially clear. What are the outputs after two clock pulses?

(d) Draw the circuit diagram and explain how to convert a MOD-16 counter to a decade counter.

2+2+(1+1)+(2+2)

7. (a) What is A/D conversion? Find the output voltage from a 5-bit ladder that has a digital input of 11101.

[Take state 0 = 0V, State 1 = +10V.]

(b) Write at least two differences between RAM and ROM.

(c) Implement the following Boolean function using Programmable Logic Array (PLA).

$$F = A + \bar{C}B.$$

(2+3)+2+3